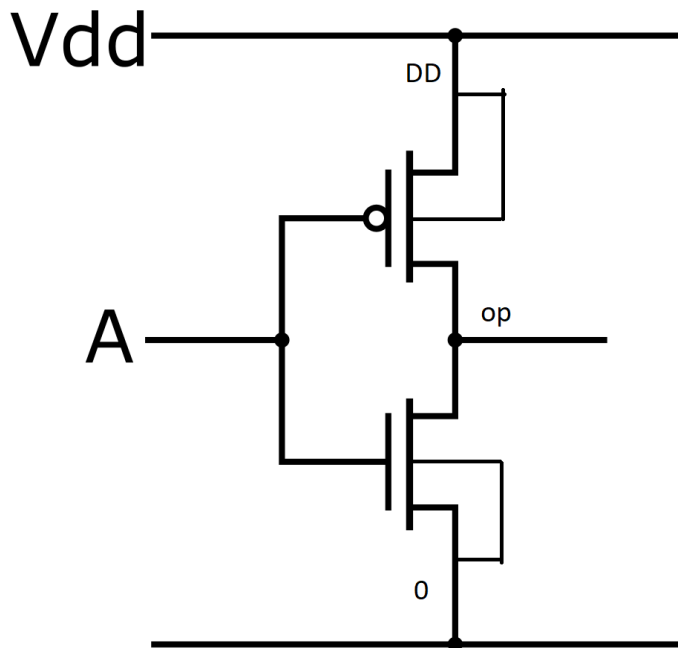


<Expt. No. 1a - MOSFET device and CMOS inverter characterization using HSPICE	
<b>NAME :</b> S. Chandra Moulee	<b>Date :</b> 07/05/2022
<b>ROLL No.:</b> CB.EN.P2VLD21016	<b>Marks :</b> out of 10

**AIM:**

To obtain MOSFET device and CMOS inverter characterization using HSPICE

**BLOCK/CIRCUIT DIAGRAM:**

**CODE:**

\*CMOS Characteristics

.MODEL PCH PMOS LEVEL=54

.MODEL NCH NMOS LEVEL=54

MPA op A DD DD PCH L=L W=W

MNA op A 0 0 NCH L=L W=W

vdd DD 0 3

va A 0 3

.DATA d1

L	W
---	---

90n	225n
-----	------

100n	250n
------	------

120n	280n
------	------


.ENDDATA

.DC va 0 3 0.01 SWEEP DATA=d1

.plot DC V(A) V(op)

.option post

.end

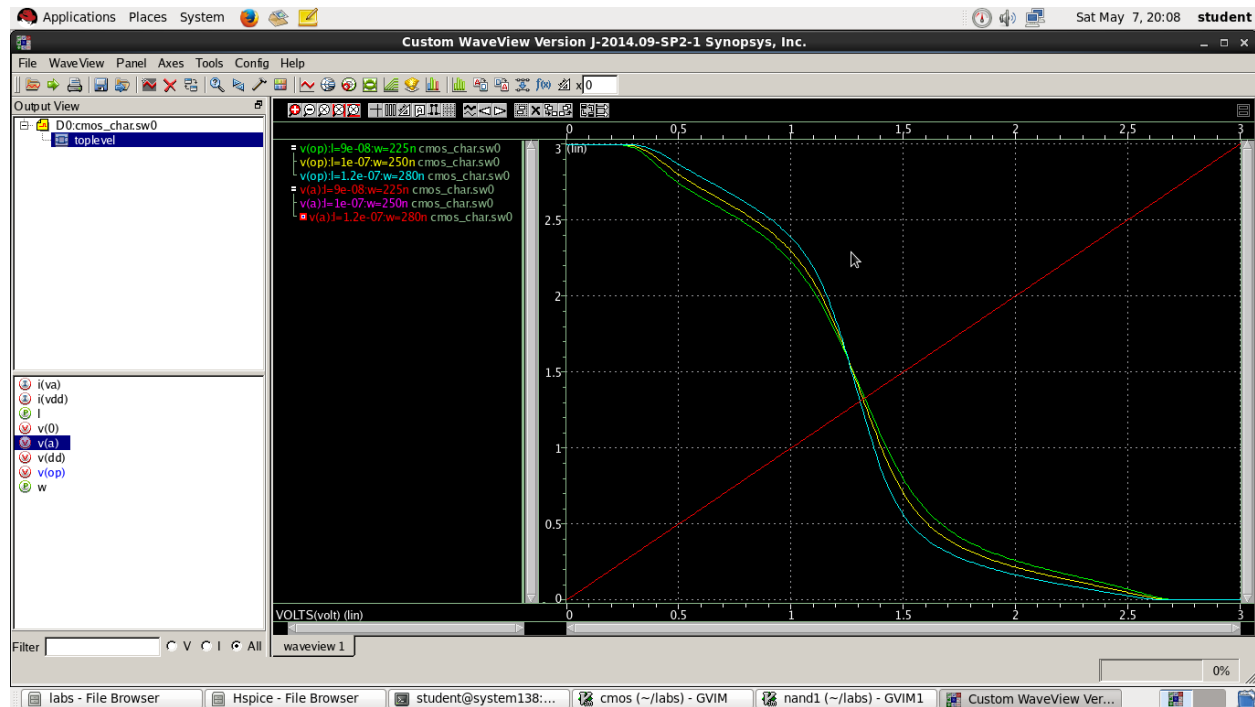**OUTPUT:****INFERENCE:**

- Analyzed the CMOS inverter characteristics using Hspice tool
- Modeled the devices only by designing netlist for the operation with level 54 devices
- Assigned node names for the MOSFET devices and provided input and analyzed the output characteristics
- Manually written the netlist for the devices, so schematic is not required
- Since node names were assigned, connections can be easily monitored
- Analyzed the output characteristics of the CMOS inverter device with three different W and L values keeping the W/L ratio as 2.5 for all W, L values respectively