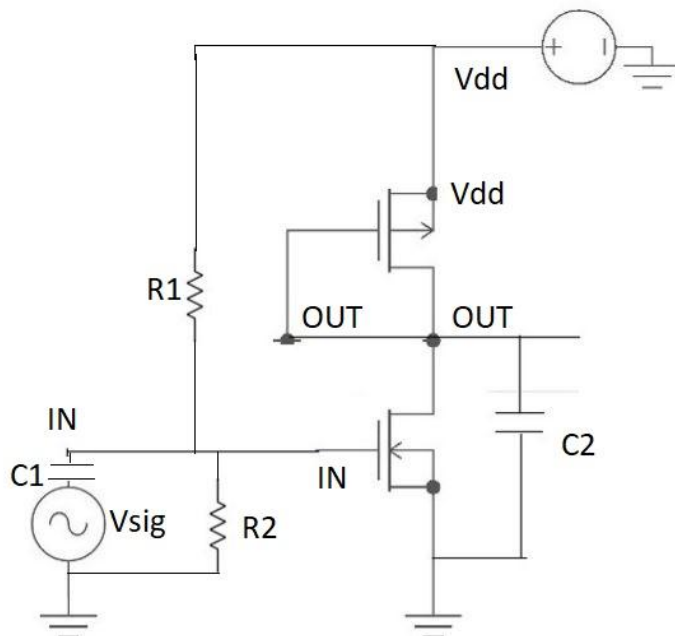


<Expt. No. 4 - Design CMOS amplifier and obtain a gain equal to the last 2 digit of roll number		
<b>NAME :</b>	S. Chandra Moulee	<b>Date :</b> 27/05/2022
<b>ROLL No.:</b>	CB.EN.P2VLD21016	<b>Marks :</b> out of 10

**AIM:**

To Design and obtain a CMOS amplifier (choose configuration on your own), the amplifier should deliver a gain equal to the last 2 digits of your roll number. With and without capacitive loads to be analyzed

**BLOCK/CIRCUIT DIAGRAM:****CODE:****CMOS Amplifier with capacitive load:**

\*AC analysis HSPICE example

```
.MODEL PCH PMOS LEVEL=54
```

```
.MODEL NCH NMOS LEVEL=54
```

```
M2 OUT IN VDD VDD PCH W=560n L=600n
```

```
M1 OUT IN 0 0 NCH W=250n L=570n
```

```
C1 VSIG IN 1u
```

CL OUT 0 10p

R1 VDD IN 6k

R2 IN 0 6k

VDC VDD 0 DC 1.5

VAC VSIG 0 AC 0.01

.AC DEC 5 0.001 2000MEG

.PRINT AC V(OUT)

.OPTIONS LIST NODE POST

.END

**CMOS Amplifier without capacitive load:**

\*AC analysis HSPICE example

.MODEL PCH PMOS LEVEL=54

.MODEL NCH NMOS LEVEL=54

M2 OUT IN VDD VDD PCH W=560n L=600n

M1 OUT IN 0 0 NCH W=250n L=570n

C1 VSIG IN 1u

R1 VDD IN 6k

R2 IN 0 6k

VDC VDD 0 DC 1.5



VAC VSIG 0 AC 0.01

.AC DEC 5 0.001 2000MEG

.PRINT AC V(OUT)

.OPTIONS LIST NODE POST

.END

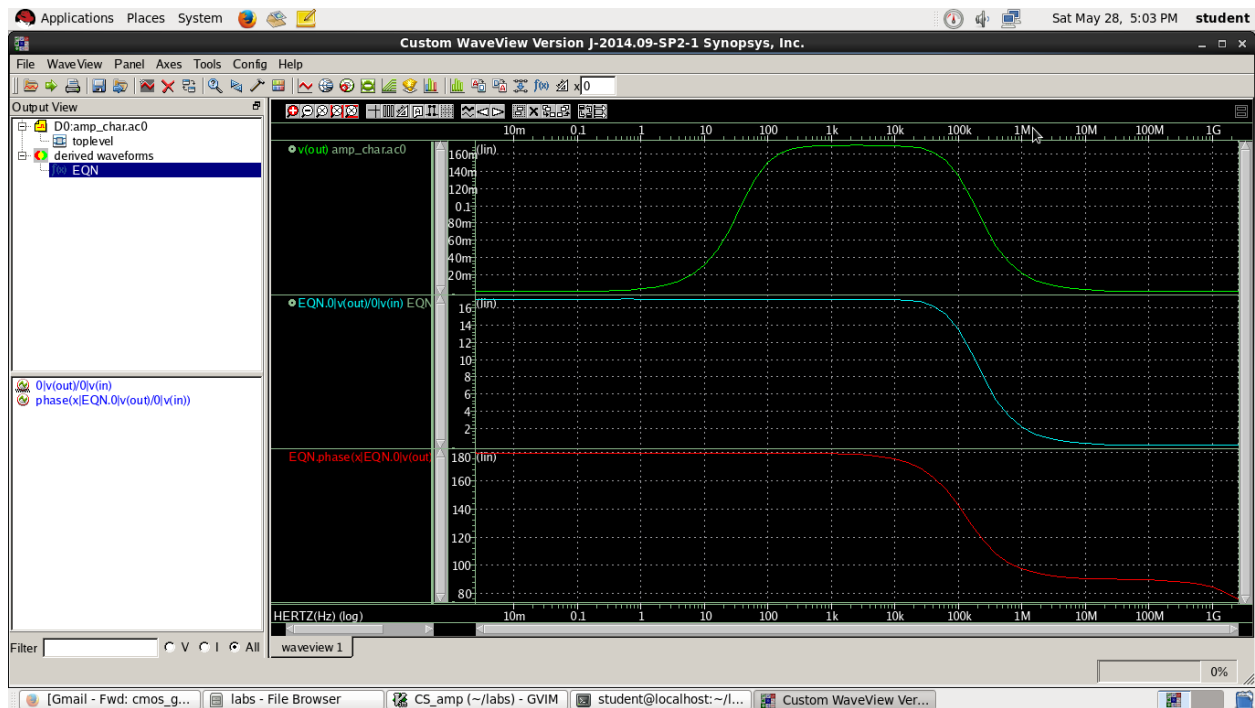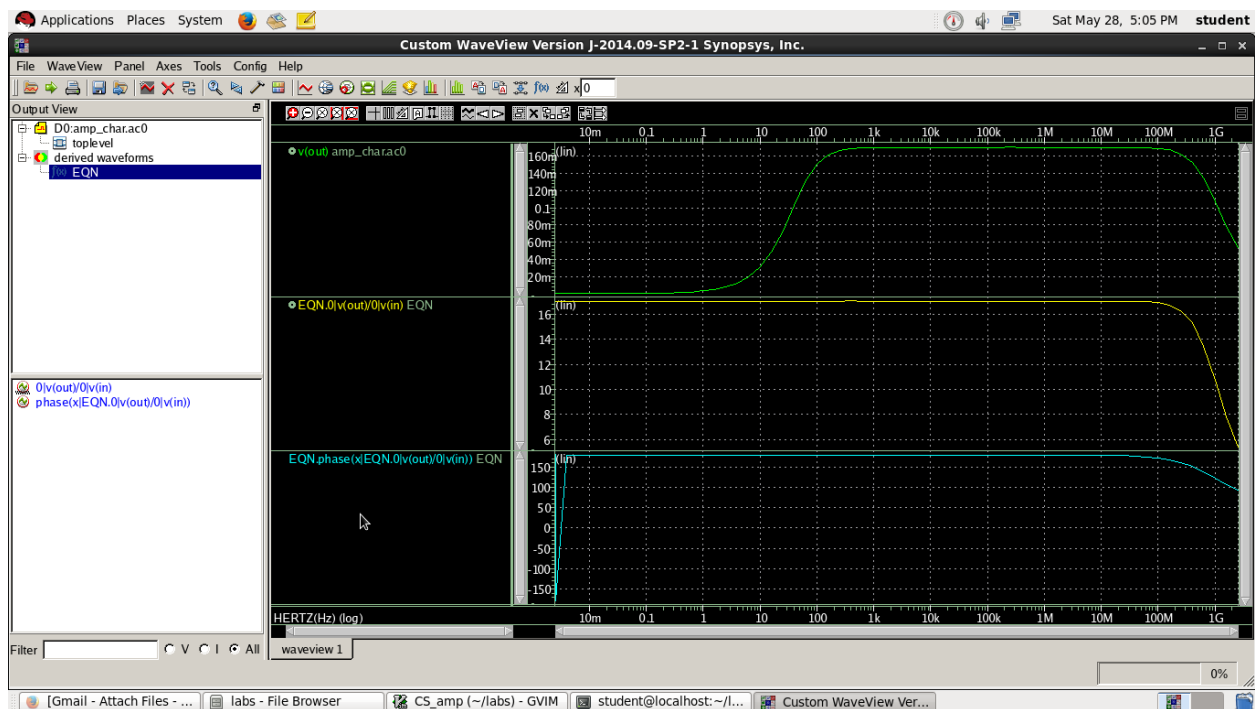**OUTPUT:****CMOS Amplifier with capacitive load:****CMOS Amplifier without capacitive load:**

**INFERENCE:**

With this experiment, we were able to obtain the gain of CMOS amplifier using HSpice tool. Here are a few things I learned from this experiment:

- Using the HSpice tool, analyzed the CMOS amplifier and obtained the gain of 16V/V.
- Manually wrote the netlist for the devices (so the schematic is not needed) in order to realize the circuit.
- Gain of the amplifier is varying by changing the W/L ratio, as the W/L ratio of NMOS increases to get the higher gain.
- Manually written the netlist for the devices, so schematic is not required
- Since node names were assigned, connections can be easily monitored
- Analyzed the output characteristics of the CMOS inverter device with three different W and L values keeping the W/L ratio as 2.5 for all W, L values respectively