 
 


<Expt. No. 2a- NAND/NOR Characteristics using HSPICE		
<b>NAME :</b> S. Chandra Mulee		<b>Date :</b> 07/08/2022
<b>ROLL No.:</b> CB.EN.P2VLD21016		<b>Marks :</b> out of 10

**AIM:**

To Obtain the CMOS NAND/NOR characteristics for three different aspect ratios and compare the characteristics using HSPICE

**BLOCK/CIRCUIT DIAGRAM:****NAND Gate:****NOR Gate:**

**CODE:****NAND Gate:**

\*NAND gate

.MODEL PCH PMOS LEVEL=54

.MODEL NCH NMOS LEVEL=54

MPA op A DD DD PCH L=L W=W

MPB op B DD DD PCH L=L W=W

MNA op A S S NCH L=L W=W

MNB S B 0 0 NCH L=L W=W

vdd DD 0 3

va A 0 3

vb b 0 2

.DC vb 0 3 0.1 SWEEP DATA=d1

.DATA d1

L        W

90n     225n

100n    250n

120n    280n

.ENDDATA

.plot DC V(va) V(vb) V(op)

.option post

.end

**NOR Gate:**

\*NOR gate

.MODEL PCH PMOS LEVEL=54

.MODEL NCH NMOS LEVEL=54

MPA D A DD DD PCH L=L W=W

MPB op B DD DD PCH L=L W=W

MNA op A 0 0 NCH L=L W=W

```
MNB op B 0 0 NCH L=L W=W
```

```
vdd DD 0 3
```

```
va A 0 0
```

```
vb b 0 2
```

```
.DC vb 0 3 0.01 SWEEP DATA=d1
```

```
.DATA d1
```

```
L      W
```

```
90n    225n
```

```
100n   250n
```

```
120n   280n
```

```
.ENDDATA
```


```
.plot DC V(A) V(B) V(op)
```


```
.option post
```

```
.end
```

## OUTPUT:

### NAND Gate:

 

 **NOR Gate:****INFERENCE:**

- Analyzed the NAND and NOR characteristics implemented using CMOS using HSPICE tool
- Modeled the devices only by designing netlist for the operation
- Assigned node names for the MOSFET devices and provided input and analyzed the output
- Manually written the netlist for the devices, so schematic is not required
- Since node names were assigned, connections can be easily monitored
- Transistor sizing is provided based on the series and parallel connections of MOSFETs
- Analyzed the output characteristics of NAND and NOR with three different aspect ratios